

SOLUTIONS TUT. SHEET # 10

Q1.

Solution Let us consider the two corner voltages V_1 and V_1' that appear on the positive side of the waveform indicated in Fig. 2.8. This waveform represents the response of the high-pass filter when RC is very large compared to T . We can write that

$$V_1' = V_1 e^{-T/2RC}$$

$$V_2' = V_2 e^{-T/2RC}$$

$$V_1 - V_2' = V$$

$$V_1' - V_2 = V$$

(1)

We can write another two equations due to the symmetry of the waveform.

$$V_1 = -V_2 \quad \text{and} \quad V_1' = -V_2'$$

$$V_1 - V_2' = V$$

Substituting for V_2' , we have

$$V_1 - V_2 e^{-T/2RC} = V$$

$$V_1 - (V_1' - V) e^{-T/2RC} = V$$

$$V_1 - (V_1 e^{-T/2RC} - V) e^{-T/2RC} = V$$

$$V_1(1 - e^{-T/2RC}) = V(1 - e^{-T/2RC})$$

When $x \ll 1$, we can write $e^{-x} \approx (1 - x)$ and $(1 - x)^{-1} \approx (1 + x)$. This relationship can be used when $T/2RC \ll 1$.

We can write

$$V_1 = \frac{V(1 - e^{-T/2RC})}{(1 - e^{-T/2RC})} = \frac{V}{(1 + e^{-T/2RC})} \quad (2)$$

Similarly we can also obtain that

$$V_1' = V_1 e^{-T/2RC} = \frac{V e^{-T/2RC}}{(1 + e^{-T/2RC})} = \frac{V}{(1 + e^{+T/2RC})} \quad (3)$$

Q2.

$$(a) V_1' = V_1 e^{-T_1/RC} = V_1 e^{-0.1/0.2} = 0.606V_1$$

$$V_2 = V_1' - V = V_1' - 1 = 0.606V_1 - 1$$

$$V_2' = V_2 e^{-T_2/RC} = V_2 e^{-0.2/0.2} = 0.367V_2$$

$$V_1 = V_2' + V = V_2' + 1 = 0.367V_2 + 1$$

We obtain the following values by solving the four equations.

$$V_1 = 0.816 \text{ V}, V_1' = 0.496 \text{ V}, V_2 = -0.504 \text{ V} \text{ and } V_2' = -0.184 \text{ V}.$$

(b) Let positive area be A_1 , and negative area be A_2 .

$$A_1 = \int_0^{0.1} 0.816 e^{-t/0.2} dt = (-0.816(0.2) e^{-t/0.2})_0^{0.1} = 0.06 \text{ V-s}$$

$$A_2 = \int_0^{0.2} (-0.504) e^{-t/0.2} dt = (0.504(0.2) e^{-t/0.2})_0^{0.2} = -0.06 \text{ V-s}$$

$$A_1 + A_2 = 0.06 + (-0.06) = 0$$

The net area is obviously zero. This means that the series capacitor blocks the dc component of the input waveform.

Q3.

Solution The peak-to-peak amplitude of the symmetrical square-wave V is given as 2 V. We know that for a symmetrical square-wave, the average value is zero.

The waveform is transmitted through an RC low-pass filter. The rising portion of the output waveform is given by Eq. (2.52).

$$v_{o1}(t) = V' + (V_1 - V')e^{-t/RC} \quad (1)$$

We are dealing with a symmetrical square-wave with zero average value. We are given that $V' = -V'' = 1 \text{ V}$. Let us assume that $T_1 = T_2 = t_p$. Substituting this in Eq. (1), we have

$$V = 1 + (-1 - V) e^{-t_p/RC}$$

$$V = 1 + (-1 - V)e^{-1} = 1 - (1 + V)(0.368)$$

$$1.368V = 0.632$$

$$V = \frac{0.632}{1.368} = 0.463 \text{ V}$$

Peak-to-peak voltage of the output is 2V that is equal to

$$v_o(\text{peak}) = 2V = 2 \times 0.463 = 0.926 \text{ V}$$

Q4.

Solution In the case of a symmetrical square waveform, we have $T_1 = T_2 = T/2$ and $V' = -V'' = V/2$. We also observe that $V_1 = -V_2$ due to symmetry. Substituting these values in Eqs (2.52) and (2.53), we can write

$$V_2 = \frac{V}{2} + \left(V_1 - \frac{V}{2} \right) e^{-T/2RC}$$

Since we know that $V_1 = -V_2$, we can write

$$V_2 = \frac{V}{2} + \left(-V_2 - \frac{V}{2} \right) e^{-T/2RC}$$

$$V_2(1 + e^{-T/2RC}) = \frac{V}{2}(1 - e^{-T/2RC})$$

$$V_2 = \frac{V(1 - e^{-T/2RC})}{2(1 + e^{-T/2RC})}$$

Multiplying the numerator and denominator in the above equation with $e^{T/2RC}$, we have

$$V_2 = \frac{V(e^{T/2RC} - 1)}{2(e^{T/2RC} + 1)}$$

If we introduce $x = T/4RC$, the above equation assumes a simple form as


$$V_2 = \frac{V(e^{2x} - 1)}{2(e^{2x} + 1)}$$

$$V_2 = \frac{V(e^x - e^{-x})}{2(e^x + e^{-x})}$$

$$V_2 = \frac{V(e^x - e^{-x})/2}{2(e^x + e^{-x})/2} = \frac{V \sinh x}{2 \cosh x}$$

$$V_2 = \frac{V}{2} \tanh x$$

Q5

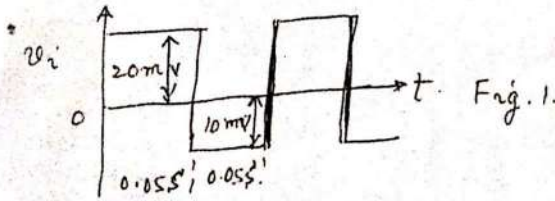

Here with $v_0 = 20\text{ mV}$, $RC = 0.47\text{ s}$.

$$v_0' = 20 \times 10^{-3} e^{-\frac{0.05}{0.47}} = 6.9 \times 10^{-3}$$

$$v_0' - v_{02} = 30 - 6.9 = 23.1\text{ mV}$$

$$v_{02}' = v_{02} e^{-t/RC} = v_{02} \times 0.345$$

$$\therefore e^{-t/RC} = e^{-\frac{0.05}{0.47}} = 0.345$$


$$v_{02}' = 7.96\text{ mV}$$

$$\therefore v_1 = 30 - 7.96 = 22.04\text{ mV}$$

$$v_1' = 22.04 \times 0.345 = 7.6\text{ mV}$$

$$\therefore v_2 = 30 - 7.6 = 22.4\text{ mV}$$
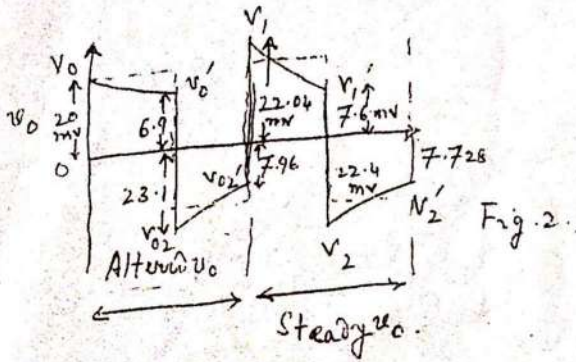
$$\therefore v_2' = 22.4 \times 0.345 = 7.728\text{ mV}$$



After a few cycles v_2' stabilizes to 7.6 mV . The required v_o is the steady v_o shown in Fig. 2

Q6. & Q7 These are theoretical questions (Given in the Book Milliman & Taub)